

Programming af Mobile Robotter

RB1-PMR – Module 8: Logic Gates


Agenda

- Recap of last module
- Logic gates
 - NOT, AND, OR, NAND, NOR, XOR, XNOR
- Combinational Logic Circuits
 - Logic diagram
 - Truth Table
 - Boolean expression
 - Common examples
 - Multiplexers, decode/encoder, full adder
- The Laws of Boolean Algebra
 - How to simplify logic circuits?
- **Next modules**
 - **Next:** Data communication (and Mini Project)
 - Q/A's? (2 modules + Mini Project work)
 - **Remember:** Fokusgruppeinterview (25/11, 8.15 - 9.15)

Week	Date	Schedule	Location	Module	Content
36	04-09-2024	08:15 - 12:00	U180	1	Introduction to the course
37	09-09-2024	08:15 - 12:00	U167	2	Basic programming concepts using Python (PA 1)
38	16-09-2024	08:15 - 12:00	U167	3	Basic IO programming using MicroPython (Portfolio 1)
39	KiCad course (Semesterprojekt i grundlæggende styring af robotter)				
40	30-09-2024	08:15 - 12:00	U167	4	Actuator interface and Object-Oriented Programming (PA 2)
41	07-10-2024	08:15 - 12:00	U167	5	Drive System designs and Multitasking (Portfolio 2)
42	Autumn vacation				
43	21-10-2024	08:15 - 12:00	U167	6	Sensors and Robot Behaviors (PA 3)
44	28-10-2024	08:15 - 12:00	U167	7	Debugging, data collection, and visualization (Portfolio 3)
45	04-11-2024	08:15 - 12:00	U167	8	Logic Gates
46	11-11-2024	08:00 - 12:00	U167	9	Data Communication (Portfolio 4: Mini Project)
47	18-11-2024	08:00 - 12:00	U167	10	Mini project work (and Q/A)
48	25-11-2024	08:00 - 12:00	U167	11	Fokusgruppeinterview and Mini project work (and Q/A)
50	02-12-2024	08:00 - 12:00	U181	12	Mini project presentation (PA 4)

Recap



- Troubleshooting and Debugging Techniques (continued)
 - Best-practice
 - Basic debugging using Python
 - LED and GPIO for Debugging
 - Data Logging using MicroPython
- Data collection using a Microcontroller
 - Types of data collect
 - End-to-end data collection (design)
 - **Define the objective**
 - **Design the data collection method**
 - **Testing and collect the data**
 - **Analyze and Interpret the Data**
- Visualization of data measurements
 - ...using Matplotlib
- Portfolio 3: Data collection of sensors
 - Q/A?
 - ...consider storing everything on a container (module 2)
 - ...when done with the test, write everything to

 

Logic Gates


CPU (Central Processing Unit) [module 1]:

  - The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - **Registers**
 - **Memory**




CPU (Central Processing Unit) [module 1]:

 - The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - **Registers**
 - **Memory**
 -all build on logic gates...



 
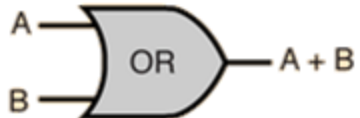


Problem
Algorithm
Program/Language
System Software
SW/HW Interface
Micro-architecture
Logic
Devices
Electrons



Logic gates

*“Is a device which accepts one or more **TRUE (1)** or **FALSE (0)** inputs and produces a **TRUE (1)** or **FALSE (0)** output according to a logical rule.”*


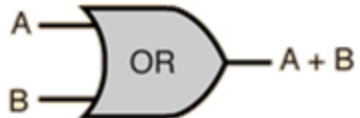


- **Binary numbers (Module 1)**
 - ...are expressed using only two digits: 0 and 1.

Example: Different basic logic gates	
AND	OR
	
NAND	NOR
	

Logic gates

*“Is a device which accepts one or more **TRUE (1)** or **FALSE (0)** inputs and produces a **TRUE (1)** or **FALSE (0)** output according to a logical rule.”*


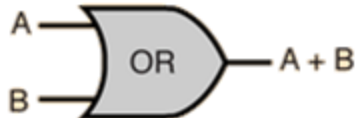


- **Binary numbers (Module 1)**
 - ...are expressed using only two digits: 0 and 1.
- **Logic gates:** Low-level basic building blocks of digital systems.
 - Input: TRUE (1) or FALSE (0)
 - Output: TRUE (1) or FALSE (0)

Example: Different basic logic gates	
AND 	OR 
NAND 	NOR 

Logic gates

*“Is a device which accepts one or more **TRUE (1)** or **FALSE (0)** inputs and produces a **TRUE (1)** or **FALSE (0)** output according to a logical rule.”*

- **Binary numbers (Module 1)**
 - ...are expressed using only two digits: 0 and 1.
- **Logic gates:** Low-level basic building blocks of digital systems.
 - Input: TRUE (1) or FALSE (0)
 - Output: TRUE (1) or FALSE (0)
- **Combinational Logic Circuits:** Multiple interconnected logic gates.
 - ...for performing more advanced operations by combining the outputs of individual gates...
 - ..eg. encoders, full adder, memory, CPU, etc.

Example: Different basic logic gates	
AND	OR
	
NAND	NOR
	

Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”



- In microcontroller: Binary digits represent voltage levels
 - (e.g., 0V for 0, 5V for 1),

Build from transistors: the most basic building block of the digital system


- Intel 8051 processor (1980) one of the first processors in the market has 50,000 transistor in it.
- Apple M1 Max processor (2021) has more than 57,000,000,000 transistors

“Acceptable” input signal voltages = TRUE/High or FALSE/Low

Acceptable TTL Gate
Input Signal Levels

  


Acceptable TTL Gate
Output Signal Levels

 


Example: Different basic logic gates (transistor switches)


AND

 


OR

 

NAND

 

NOR

 


Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”

- **Buffer**

- One input
- Outputs its input

 

Input	Output
A	Q
0	0
1	1

Logic gates


“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”

- **Buffer**


- One input
- Outputs its input

- **Inverting buffer** (Inverter / NOT gate)

 
- One input
- Outputs the opposite of its input
- **Inversion:** Marked with a dot



7404

 

Input	Output
A	Q
0	0
1	1

 

Input	Output
A	Q
0	1
1	0


Symbols




Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”

 - **Buffer**
 - One input
 - Outputs its input
- **Inverting buffer** (Inverter / NOT gate)
 - One input
 - Outputs the opposite of its input
 - **Inversion:** Marked with a dot



Input	Output
A	Q
0	0
1	1

 

Input	Output
A	Q
0	1
1	0

Truth table

“Shows what is the logic output of the circuit for each possible input”

Symbols




Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”


- **AND Gate**

 - The AND operation is done on at least two inputs
- The AND operation on A and B represented as A.B
 - Outputs only TRUE is all inputs are TRUE
 - **Example:** Q=1 if A AND B are 1



A AND B

Input		Output
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

 


Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”


• OR Gate

 - The OR operation is done on at least two inputs
- The OR operation on A and B represented as $A+B$
 - Outputs TRUE is one of the inputs are TRUE
 - Only outputs FALSE if all inputs are FALSE
- **Example:** $Q=1$ if A OR B are 1



A OR B

Input		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

 

7432 Quad 2 Input OR

Logical Operators (Module 2)


- Used for combining conditions with logical operators (returns either True or False)
 - Commonly in **conditional statements** and **loops**.

a	b	a and b	a or b	not a and b	not (a and b)
True	True	True	True	False	False
True	False	False	True	False	True
False	True	False	True	True	True
False	False	False	False	False	True


Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”

 - **NAND Gate (Not AND)**
 - The inverse of the AND gate.
 - Outputs TRUE unless all its inputs are TRUE.





NAND		
Input		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

 


Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”

  
- **NAND Gate (Not AND)**
 - The inverse of the AND gate.
 - Outputs TRUE unless all its inputs are TRUE.
- **NOR Gate (Not OR)**
 - The inverse of the OR gate.
 - Outputs TRUE only if all its inputs are FALSE.



NAND		
Input		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

 


NOR		
Input		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

 

NAND		
Input		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

(Combinational Logic Circuits?)

 


NOR		
Input		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Logic gates


“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”

- **XOR Gate (Exclusive OR)**

 - Outputs TRUE if its inputs are different.
 - one is FALSE and the other is TRUE





XOR		
Input		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

 

Logic gates

“Is a device which accepts one or more TRUE (1) or FALSE (0) inputs and produces a TRUE (1) or FALSE (0) output according to a logical rule.”

  - XOR Gate (Exclusive OR)
 - Outputs TRUE if its inputs are different.
 - one is FALSE and the other is TRUE
- XNOR Gate (Exclusive NOR)
 - The inverse of the XOR gate.
 - Outputs TRUE if its inputs are the same.
 - Both has to either FALSE or TRUE



XOR		
Input		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0



XNOR		
Input		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

Combinational Logic Circuits

Combinational Logic Circuits

“Built using multiple basic logic gates like AND, OR, NOT, NAND, NOR, XOR, and XNOR.”

- **Combining logic gates** in various ways to implement specific functions.

The three main ways of specifying the function of a combinational logic circuit are:


Combinational Logic Circuits

“Built using multiple basic logic gates like AND, OR, NOT, NAND, NOR, XOR, and XNOR.”

- **Combining logic gates** in various ways to implement specific functions.

The three main ways of specifying the function of a combinational logic circuit are:

 - **Logic Diagram:** A graphical representation of a logic circuit.
 - Shows the wiring and connections of each individual logic gate, represented by a specific graphical symbol, that implements the logic circuit.




Combinational Logic Circuits

“Built using multiple basic logic gates like AND, OR, NOT, NAND, NOR, XOR, and XNOR.”

- **Combining logic gates** in various ways to implement specific functions.

The three main ways of specifying the function of a combinational logic circuit are:

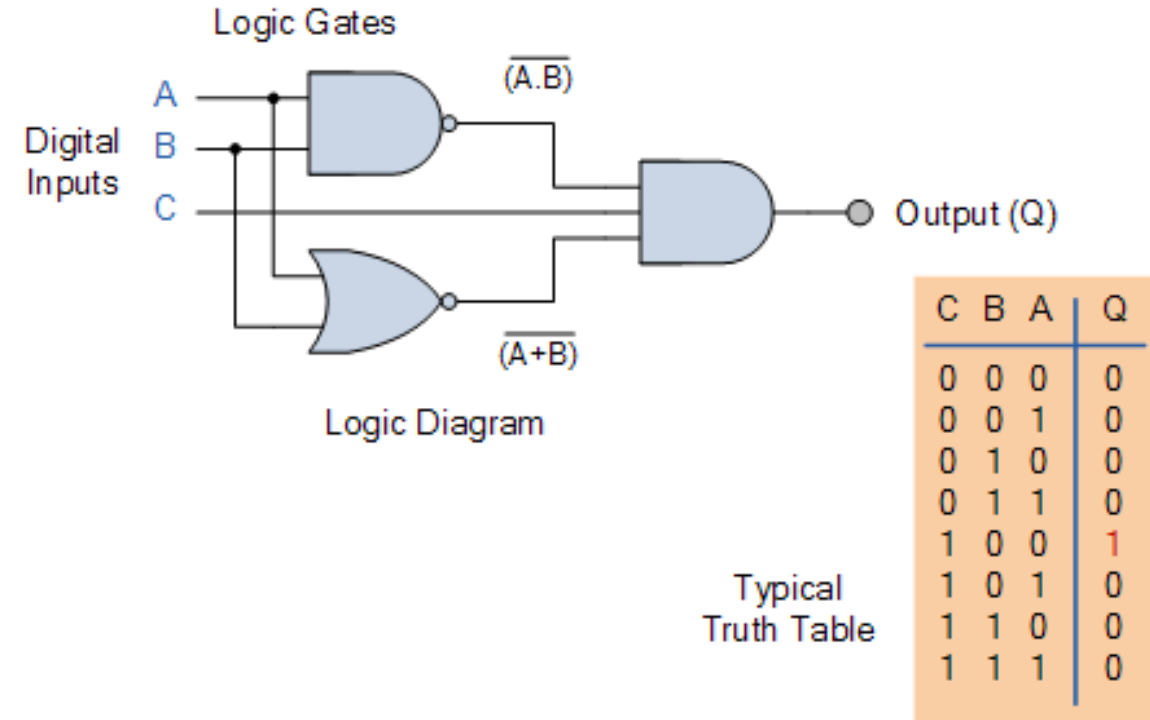- **Logic Diagram:** This is a graphical representation of a logic circuit.
- **Truth Table:** A concise list that defines all the output states in tabular form.
 - ...for each possible combination of input variable that the gate could encounter.




Combinational Logic Circuits

“Built using multiple basic logic gates like AND, OR, NOT, NAND, NOR, XOR, and XNOR.”

- **Combining logic gates** in various ways to implement specific functions.

The three main ways of specifying the function of a combinational logic circuit are:

- **Logic Diagram:** This is a graphical representation of a logic circuit.
- **Truth Table:** A concise list that defines all the output states in tabular form.
- **Boolean expression:** A mathematical/algebraic expression showing the operation of the logic circuit for each input variable
 - Each variable is a logic value (either True or False)
 - ...and results in a logic output (either True or False)

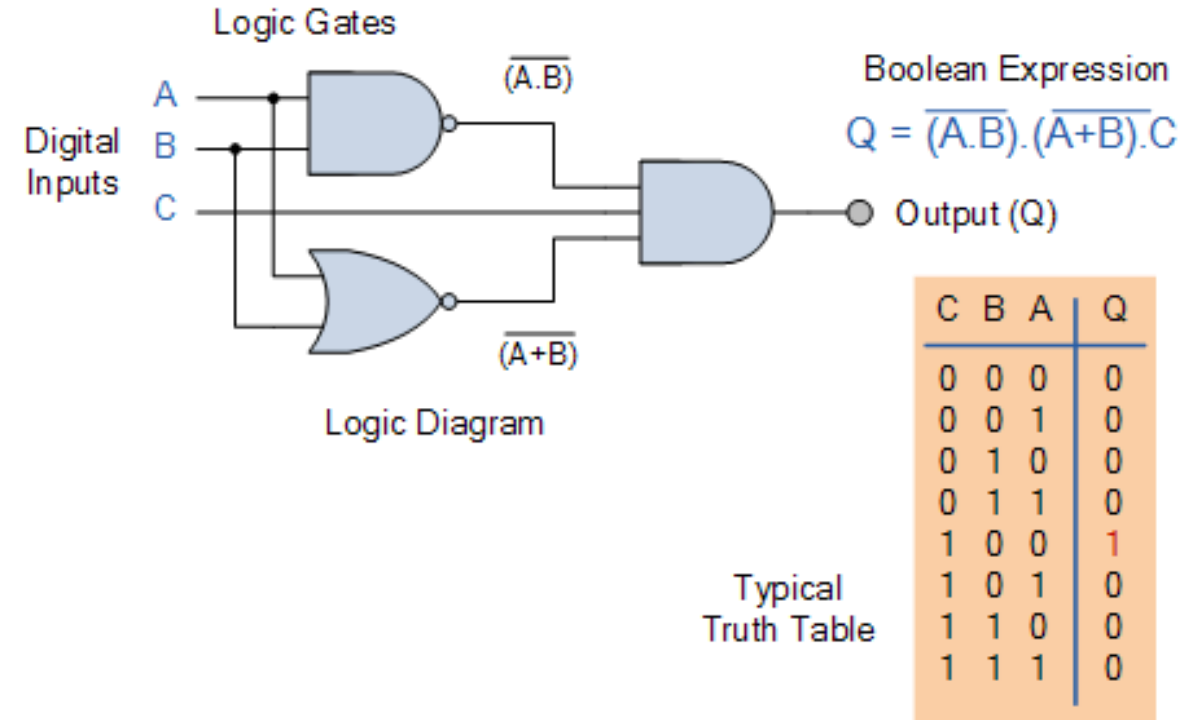


Combinational Logic Circuits

“Built using multiple basic logic gates like AND, OR, NOT, NAND, NOR, XOR, and XNOR.”

- **Boolean algebra expressions and functions**
 - Symbols / “Syntax”
 - ...different symbols, same functionalities

Logical connectives	
NOT	$\neg A, \neg A, \overline{A}, \sim A$
AND	$A \wedge B, A \cdot B, AB, A \& B, A \& \& B$
NAND	$A \overline{\wedge} B, A \uparrow B, A \mid B, \overline{A \cdot B}$
OR	$A \vee B, A + B, A \mid B, A \parallel B$
NOR	$A \overline{\vee} B, A \downarrow B, \overline{A + B}$
XNOR	$A \text{ XNOR } B$
≡ equivalent	$A \equiv B, A \Leftrightarrow B, A \Leftrightarrow B$
XOR	$A \vee B, A \oplus B$
≠ nonequivalent	$A \not\equiv B, A \nLeftrightarrow B, A \nLeftrightarrow B$
implies	$A \Rightarrow B, A \supset B, A \rightarrow B$
converse	$A \Leftarrow B, A \subset B, A \leftarrow B$

Function	Description	Expression
1.	Null	0
2.	Identity	1
3.	Input A	A
4.	Input B	B
5.	NOT A	\overline{A}
6.	NOT B	\overline{B}
7.	A (AND) B	$A \cdot B$
8.	A (AND) [B (NOT)]	$A \cdot \overline{B}$
9.	[(NOT) A] (AND) B	$\overline{A} \cdot B$
10.	(NOT) [A (AND) B]	$\overline{A \cdot B}$
11.	A (OR) B	$A + B$
12.	A (OR) [B (NOT)]	$A + \overline{B}$
13.	[(NOT) A] (OR) B	$\overline{A} + B$
14.	(NOT) [A (OR) B]	$\overline{A + B}$
15.	Exclusive-OR	$A \cdot \overline{B} = \overline{A} \cdot B$
16.	Exclusive-NOR	$A \cdot B + \overline{A} \cdot \overline{B}$

 

C	B	A	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

Typical Truth Table


Illustration: https://www.electronics-tutorials.ws/combinational/comb_1.html
<https://www.electronics-lab.com/article/laws-of-boolean-algebra/>
https://en.wikipedia.org/wiki/Boolean_function

Example: Implementation of Boolean Algebra

- Can be implemented by interconnection of logic gates:
 - $F = \overline{AB} + \bar{B}C$

 Example: Implementation of Boolean Algebra


- Can be implemented by interconnection of logic gates:
 - $F = \overline{AB} + \overline{B}C$



Example: Implementation of Boolean Algebra

- Can be implemented by interconnection of logic gates:


- $F = \overline{A}B + \overline{B}C$

 

Example: Implementation of Boolean Algebra

- Can be implemented by interconnection of logic gates:


- $F = \overline{A}B + \overline{B}C$

 

Example: Implementation of Boolean Algebra



- Can be implemented by interconnection of logic gates:

- $F = \overline{A}B + \overline{B}C$

 

  Example: Implementation of Boolean Algebra



- Can be implemented by interconnection of logic gates:
 - $F = \overline{AB} + \bar{B}C$



Example: Implementation of Boolean Algebra

- Can be implemented by interconnection of logic gates:



- $F = \overline{A}B + \overline{B}C$

  

Example: Implementation of Boolean Algebra

- Can be implemented by interconnection of logic gates:



- $F = \overline{A}B + \overline{B}C$

  

Example: Implementation of Boolean Algebra


- Can be implemented by interconnection of logic gates:

- $F = \overline{A}B + \overline{B}C$

  

 Task: 15 min

- ? Go to <https://logic.ly/demo/>
- ? Draw the following circuit
- ? Simulate the following circuit and fill the truth table for that




A	B	C	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Combinational Logic Circuits (common examples)

Combinational Logic Circuits (Common Examples)

- **Multiplexers (MUX):** a circuit that selects one of several input signals and forwards the selected input to a single output line. It uses control signals to determine which input to pass through.
 - **Example:** 2-to-1 MUX

S	Y
0	D_0
1	D_1

 

S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Combinational Logic Circuits (Common Examples)

- **Multiplexers (MUX):** a circuit that selects one of several input signals and forwards the selected input to a single output line. It uses control signals to determine which input to pass through.

- **Example: 2-to-1 MUX**


- $S=0$

- $A \text{ AND } 1 = A$
 - $B \text{ AND } 0 = 0$
 - $A \text{ OR } 0 = A$

- $S=1$


- $A \text{ AND } 0 = 0$
 - $B \text{ AND } 1 = B$
 - $B \text{ OR } 0 = B$

S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

Combinational Logic Circuits (Common Examples)

 
- **Decoder:** a combinational logic circuit that converts binary input data into a unique output pattern.
 - A decoder has n inputs and 2^n outputs
- **Encoder:** a combinational logic circuit that performs the reverse operation of a decoder.
 - A decoder has 2^n inputs and n outputs



Combinational Logic Circuits (Common Examples)

- **Decoder:** a combinational logic circuit that converts binary input data into a unique output pattern.
 - A decoder has n inputs and 2^n outputs
- **Encoder:** a combinational logic circuit that performs the reverse operation of a decoder.
 - A decoder has 2^n inputs and n outputs
- **Example: 2-to-4 decoder**
 - Two input lines: A_0 and A_1 ,


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

Combinational Logic Circuits (Common Examples)

- **Decoder:** a combinational logic circuit that converts binary input data into a unique output pattern.
 - A decoder has n inputs and 2^n outputs
- **Encoder:** a combinational logic circuit that performs the reverse operation of a decoder.
 - A decoder has 2^n inputs and n outputs
- **Example: 2-to-4 decoder**


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

Combinational Logic Circuits (Common Examples)

- **Decoder:** a combinational logic circuit that converts binary input data into a unique output pattern.
 - A decoder has n inputs and 2^n outputs
- **Encoder:** a combinational logic circuit that performs the reverse operation of a decoder.
 - A decoder has 2^n inputs and n outputs
- **Example: 2-to-4 decoder**
 - Two input lines: A0 and A1,
 - Generates four output lines: Y0, Y1, Y2, and Y3
 - Corresponding to the truth table


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

Combinational Logic Circuits (Common Examples)

- **Decoder:** a combinational logic circuit that converts binary input data into a unique output pattern.
 - A decoder has n inputs and 2^n outputs
- **Encoder:** a combinational logic circuit that performs the reverse operation of a decoder.
 - A decoder has 2^n inputs and n outputs
- **Example: 2-to-4 decoder**
 - Two input lines: A_0 and A_1 ,
 - Generates four output lines: Y_0 , Y_1 , Y_2 , and Y_3
 - Corresponding to the truth table
 - 4x AND gates
 - 4x NOT gates


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

Task: 10 min

- ? Go to <https://logic.ly/demo/>
- ? Draw the 2 to 4 Decoder and simulate it


A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

Combinational Logic Circuits (Common Examples)

- **Full Adder:** a combinational logic circuit that adds three binary digits: two significant bits and an optional carry-in bit from a previous addition operation.
- **Inputs:**
 - **A:** First significant bit.
 - **B:** Second significant bit.
 - **Cin:** Carry-in bit from a previous addition.
- **Outputs:**
 - **Sum (S):** The sum of the three input bits.
 - **Cout (Cout):** The carry-out bit, which is the overflow bit from the sum.
- **Example:** 1-bit Full Addition

 
$$\begin{array}{r}
 a_{n-1}a_{n-2} \dots a_1a_0 \\
 b_{n-1}b_{n-2} \dots b_1b_0 \\
 \hline
 C_n C_{n-1} \dots C_1 \\
 S_{n-1} \dots S_1S_0
 \end{array}$$



Combinational Logic Circuits (Common Examples)

- **Full Adder:** a combinational logic circuit that adds three binary digits: two significant bits and an optional carry-in bit from a previous addition operation.
- **Inputs:**
 - **A:** First significant bit.
 - **B:** Second significant bit.
 - **Cin:** Carry-in bit from a previous addition.
- **Outputs:**
 - **Sum (S):** The sum of the three input bits.
 - **Cout (Cout):** The carry-out bit, which is the overflow bit from the sum.
- **Example:** 1-bit Full Addition
 - 2x XOR gate
 - 2x AND gate
 - 1x OR gate

 
$$\begin{array}{r}
 a_{n-1}a_{n-2} \dots a_1a_0 \\
 b_{n-1}b_{n-2} \dots b_1b_0 \\
 \hline
 C_n C_{n-1} \dots C_1 \\
 \hline
 S_{n-1} \dots S_1S_0
 \end{array}$$



CPU (Central Processing Unit) [module 1]:

- The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - Usually denoted with this symbol:
 - Example
 - **Registers**
 - **Memory**
 - ...all build on logic gates..


$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A – B
111	SLT

 

CPU (Central Processing Unit) [module 1]:


- The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - Usually denoted with this symbol:
 - Example
 - **Registers**
 - **Memory**
 - ...all build on logic gates..

$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT

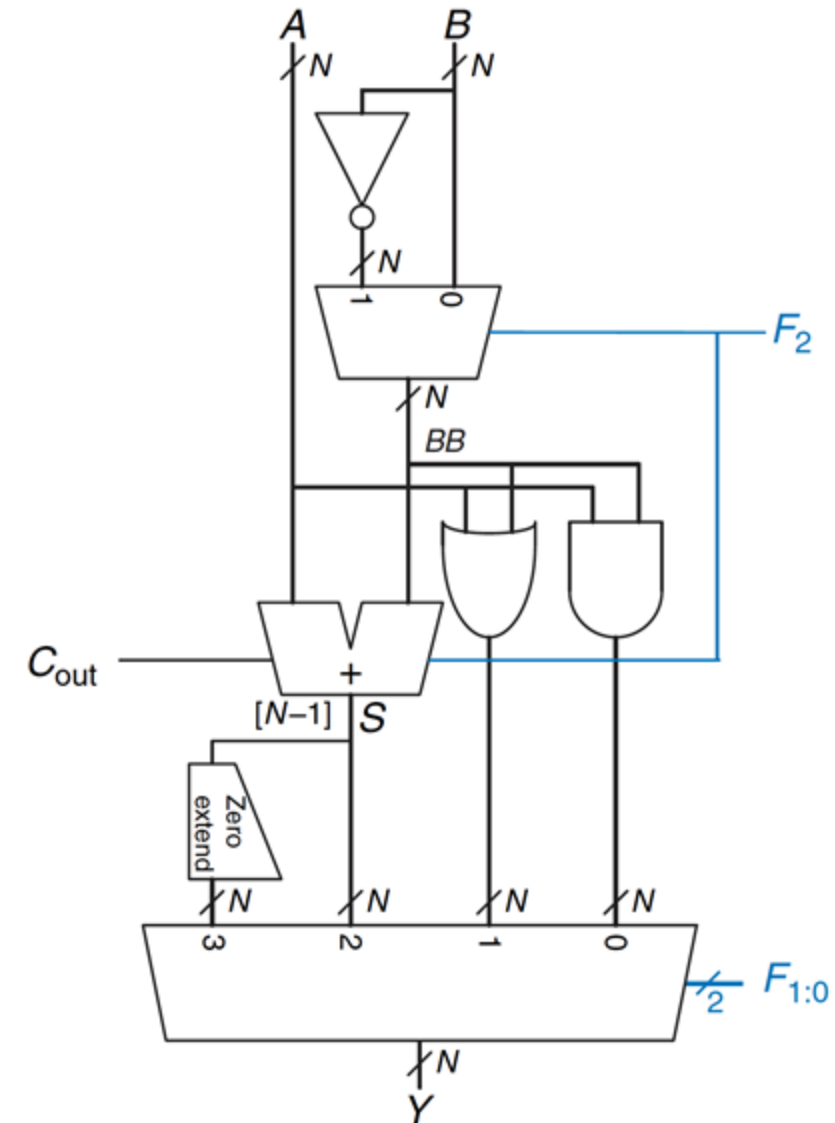

CPU (Central Processing Unit) [module 1]:

 
- The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - **Registers**
 - **Memory**



 
Task: 15 min

Simulate a Full adder

- ? Go to <https://logic.ly/demo/>
- ? Implement a one-bit full adder
- ? Fill out the truth table (on the right)
- ? Implement a 4-bit adder (as illustrated below)




A	B	C _{in}	C _{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

 

Combinational Logic Circuits (Common Examples)



- **Gated D Latch:** a type of digital storage device. It is a basic building block of flip-flops and is used to store one bit of data.
- **Inputs:**
 - **Data Input (D):** This is the input signal that the latch will store.
 - **Enable/Clock Input (CLK or EN):** This control signal determines when the data input is sampled and stored in the latch. (**Write enable**)
- **Outputs**
 - **Q Output:** The output of the latch, which represents the stored data.
 - **Q' (Q-bar) Output:** The complement of the Q output.
- **When Enable (EN/CLK) is High (1):**
 - The latch is in the "transparent" mode,
 - ...meaning the output **Q** follows the input **D**.
 - Whatever value is present on **D** is passed directly to **Q**.
 - If **D** is 1, **Q** will become 1.
 - If **D** is 0, **Q** will become 0.
- **When Enable (EN/CLK) is Low (0):**
 - The latch is in the "latched" or "hold" mode.
 - The output **Q** retains its previous state, regardless of any changes in the input **D**.
 - The stored value remains the same until the enable signal (EN/CLK) goes high again.

Input		Output
EN/CLK	D	Q
0	0	Q_{prev}
0	1	Q_{prev}
1	0	0
1	1	1

 

CPU (Central Processing Unit) [module 1]:


- The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - **Registers**
 - **Example:** a 4-bit register (data is referenced as $Q[3:0]$)
 - A single **Clock** signal for all latches for simultaneous writes
 - **Memory**
 - ...all build on logic gates..

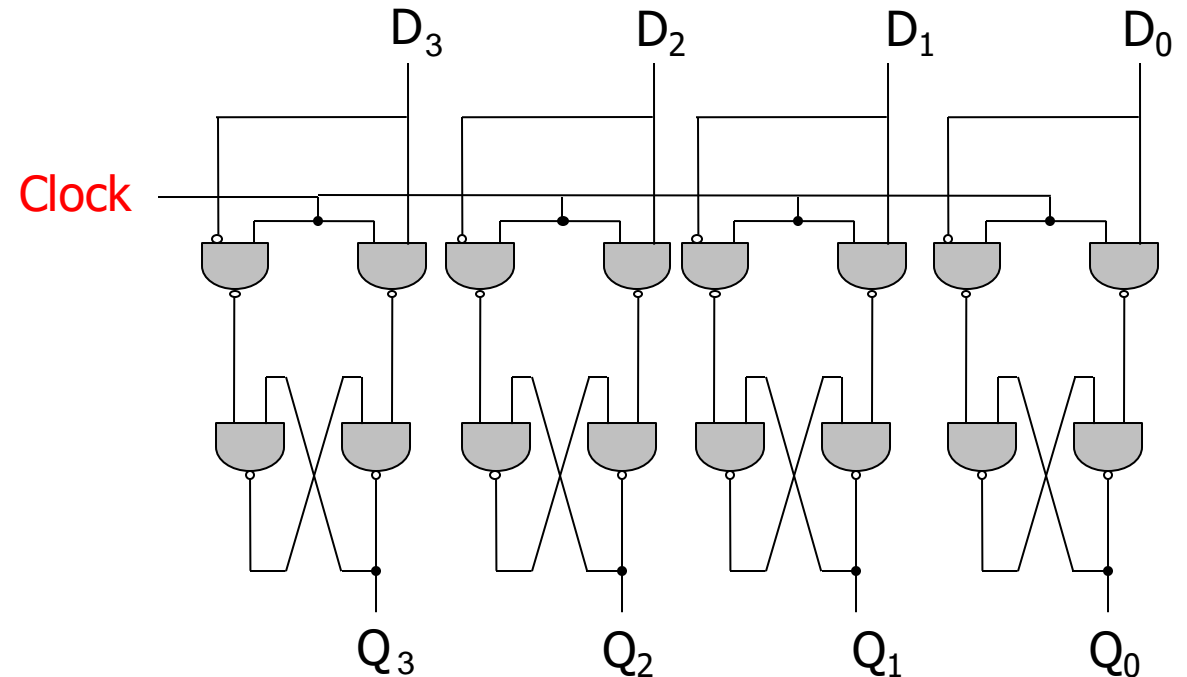 Clock

CPU (Central Processing Unit) [module 1]:

- The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - **Registers**
 - **Example:** a 4-bit register (data is referenced as $Q[3:0]$)
 - A single **Clock** signal for all latches for simultaneous writes
 - **Memory**
 - ...all build on logic gates..

Clock

 

Clock




$D_{3:0}$

4


4

$Q_{3:0}$

 


CPU (Central Processing Unit) [module 1]:

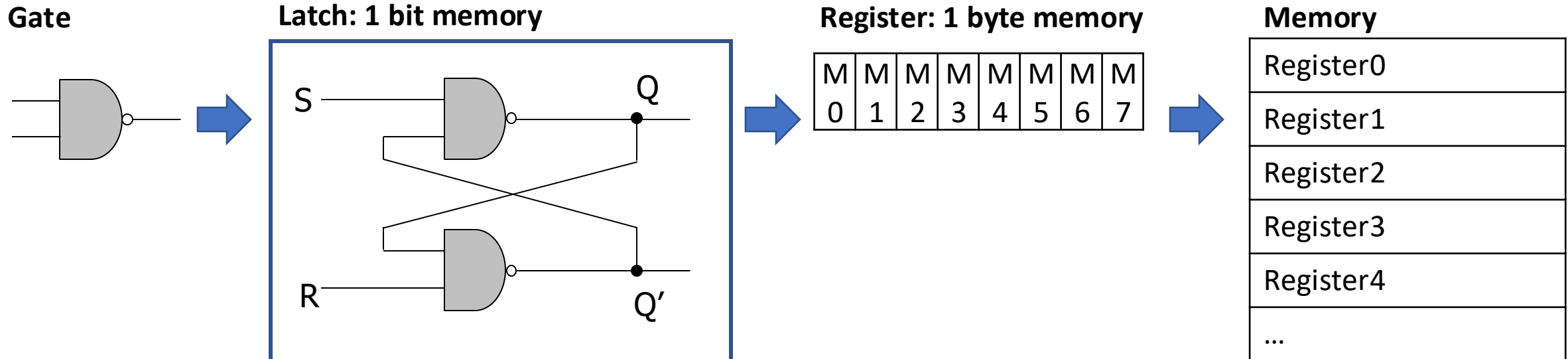- The brain of the microcontroller, responsible for executing instructions.
 - **Control Unit**
 - **Arithmetic Logic Unit (ALU)**
 - **Registers**
 - **Example:** a 4-bit register (data is referenced as Q[3:0])
 - A single **Clock** signal for all latches for simultaneous writes
 - **Memory**



Task (10 min): implement a D latch

- Go to <https://logic.ly/demo/>
- Implement and simulate one bit memory using a gated D latch

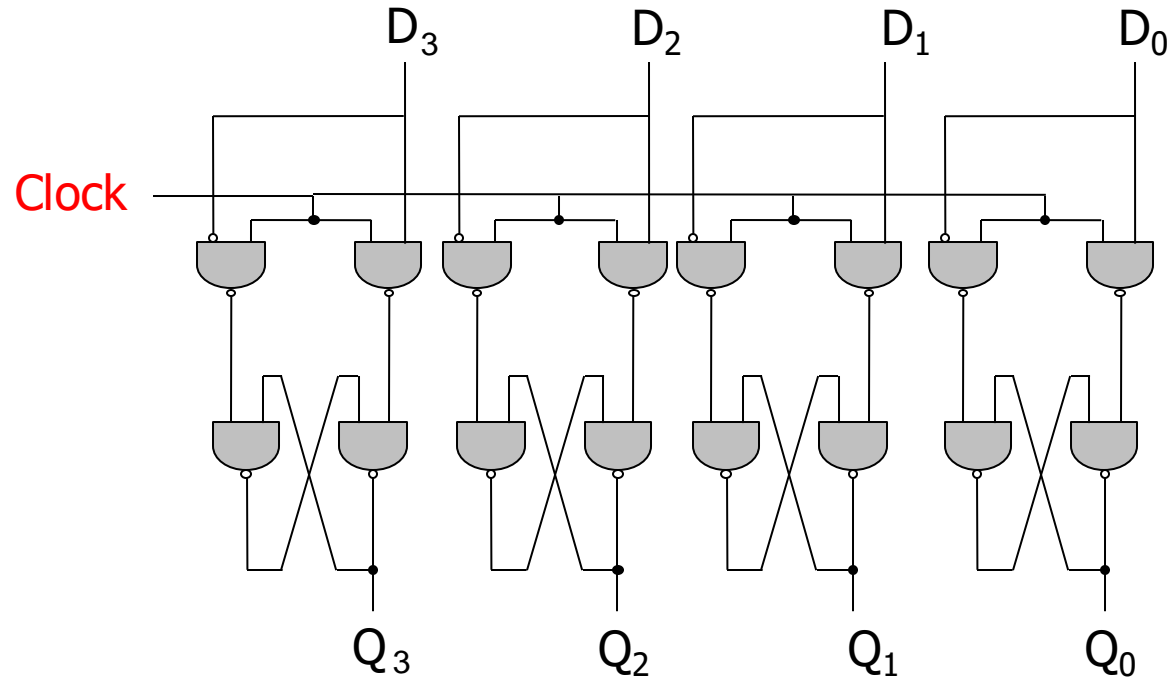
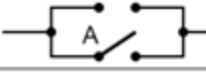
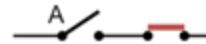
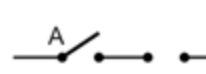
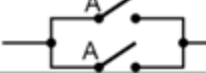
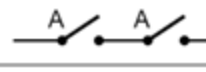
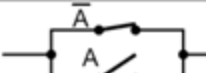
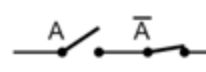
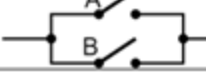
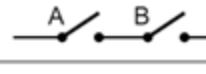


Laws of Boolean Algebra

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

- ...provide the foundational rules for simplifying logic circuits
 - **Optimization of circuit design**
 - Large logic expressions can be minimized
 - ...which translates to fewer gates in a circuit.
 - ...less gates, less heat...
 - **Increased processing speed**
 - ...fewer components, faster processing time
 - **Reliability**
 - Less components, less complexity
 - ...meaning higher reliability

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{\overline{A}}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{A}.\overline{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{A}+\overline{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Annulment laws** (Null laws)

- OR null law:
 - ...anything OR'ed with 1 is 1.
- AND null law:
 - ...anything AND'ed with 0 is 0.

(Input A has no effect)

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{\overline{A}}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{A}.\overline{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{A}+\overline{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Identity laws:**

- ...a variable retains its identity
 - when
 - ...a variable OR'ed to 1 will always yield the variable itself, or
 - ...a variable AND'ed by 1 will always yield the variable itself

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{A}.\overline{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{A}+\overline{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Identity laws:**
 - ...a variable retains its identity
- **Idempotent laws**
 - ...combining a variable with itself using an OR or AND operation yields the variable itself.

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\overline{\overline{A}}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{A}.\overline{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{A}+\overline{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Identity laws:**
 - ...a variable retains its identity
- **Idempotent laws**
 - ...combining a variable with itself using an OR or AND operation yields the variable itself.
- **Double Negation law**
 - ...a variable negated twice will return to its original value

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{\overline{A}}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{A}.\overline{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{A}+\overline{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”


- **Identity laws:**
 - ...a variable retains its identity
- **Idempotent laws**
 - ...combining a variable with itself using an OR or AND operation yields the variable itself.
- **Double Negation law**
 - ...a variable negated twice will return to its original value
- **Complement laws**
 - ... a variable OR'ed with its complement (inverse) will always yield 1, or
 - ...a variable AND'ed with its complement will always yield 0

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{B}.\overline{A}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{B}+\overline{A}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

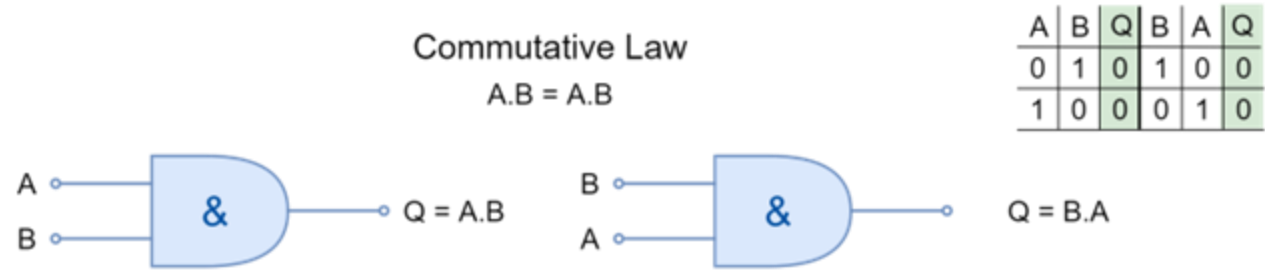- **Commutative law**
 - ...the order of variables in an OR or AND operation does not affect the result.



Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{\overline{A}}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{A}.\overline{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{A}+\overline{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Commutative law**
 - ...the order of variables in an OR or AND operation does not affect the result.
 - ...meaning, your boolean expressions to be rearranged without changing the outcome
 - Useful for
 - Simplifying expressions
 - Designing flexible logic circuits.

Commutative Law
 $A.B = A.B$

A	B	Q	B	A	Q
0	1	0	1	0	0
1	0	0	0	1	0




Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{B}.\overline{A}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{B}+\overline{A}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Commutative law**
 - ...the order of variables in an OR or AND operation does not affect the result.
- **Associative law**
 - ...grouping of variables in an OR or AND operation does not affect the result.

 Associative Law
 $A(BC) = (AB)C = (AC)B = ABC$



A	B	C	AB	BC	CA	A(BC)	(AB)C	(AC)B
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	1	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0
1	1	1	1	1	1	1	1	1

Boolean (or Switching) Algebra



Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Commutative law**
 - ...the order of variables in an OR or AND operation does not affect the result.
- **Associative law**
 - ...grouping of variables in an OR or AND operation does not affect the result.
 - ...meaning,
 - when multiple instances of the same operation are combined,
 - the order in which they are grouped can be rearranged without changing the outcome.

  Associative Law
 $A(BC) = (AB)C = (AC)B = ABC$



A	B	C	AB	BC	CA	A(BC)	(AB)C	(AC)B
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	1	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0
1	1	1	1	1	1	1	1	1

Boolean (or Switching) Algebra

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$


Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

- **Commutative law**
 - ...the order of variables in an OR or AND operation does not affect the result.
- **Associative law**
 - ...grouping of variables in an OR or AND operation does not affect the result.
- **Absorption law**
 - ...certain combinations of variables can be "absorbed" into simpler expressions.
 - ...meaning, simplifying expressions by eliminating redundant terms.
- **Distributive Law**
 - ...a variable to be distributed across an AND or OR operation.

Absorption Law

 
$$A + (A \cdot B) = (A \cdot 1) + (A \cdot B) = A(1 + B) = A$$



A	B	$A \cdot B$	Q
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

Absorption Law
 
$$A(A + B) = (A + 0) \cdot (A + B) = A + (0 \cdot B) = A$$



A	B	$A + B$	Q
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1


Boolean (or Switching) Algebra

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$


Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit.”

 - De Morgan’s Theorem (Two fundamental principles)
 - First Theorem (Change an OR to an AND)



 - Second Theorem (Change an AND to an OR)



Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \overline{\overline{A}}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\overline{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\overline{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\overline{A}.\overline{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\overline{A}+\overline{B}$	Invert and replace AND with OR		De Morgan's Theorem


SDU (Only ANDs or ORs makes it easier to simplify the expression)

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

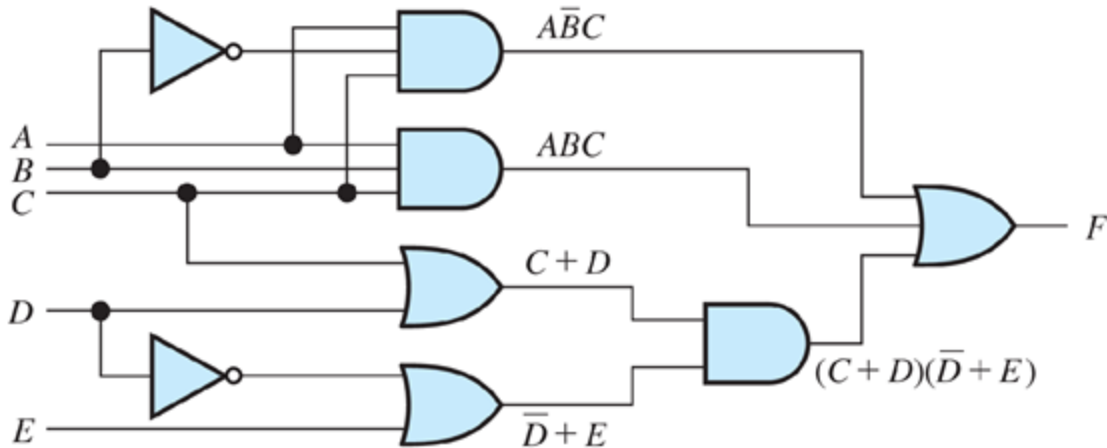- Example (complex)

$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$




Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

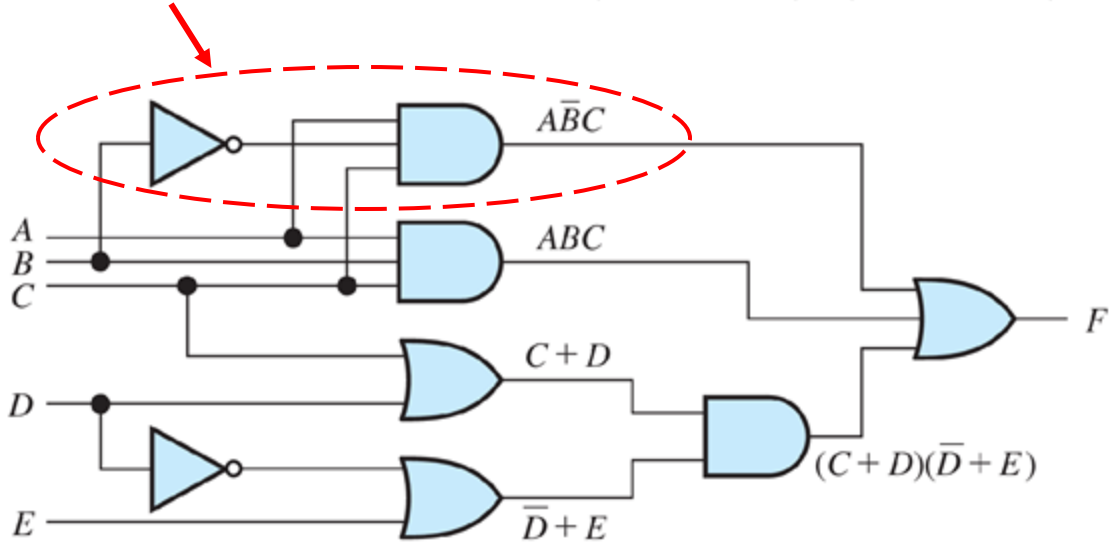- Example (complex)

$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$




Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\bar{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

- Example (complex)

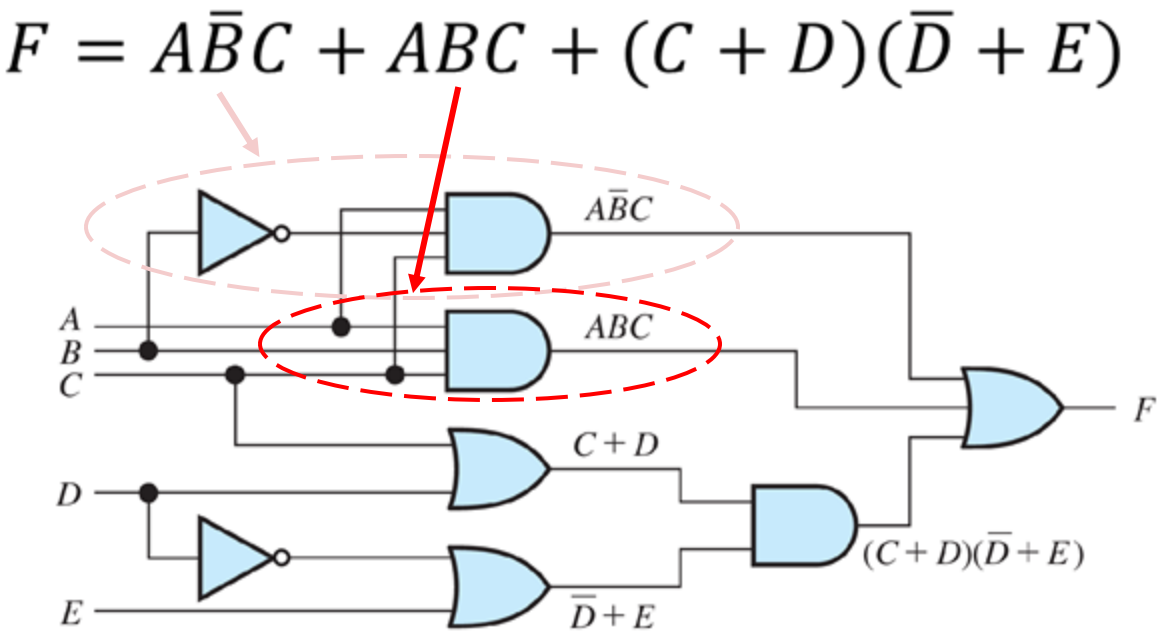


Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

- Example (complex)

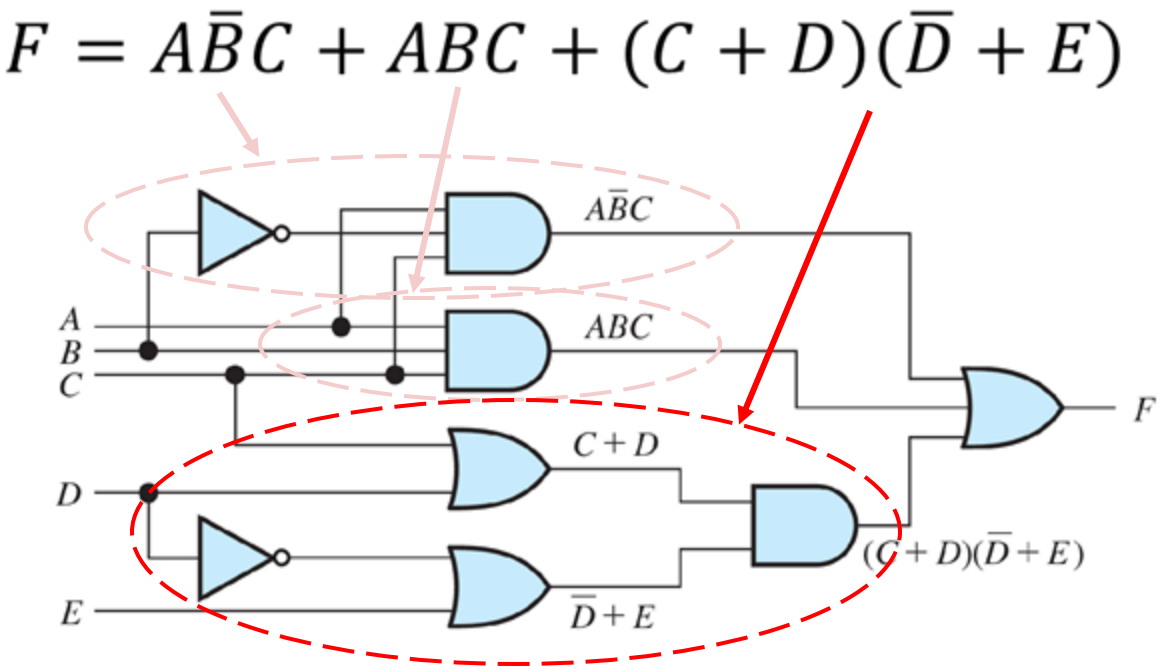


Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

 - Example (complex)

$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$




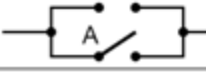
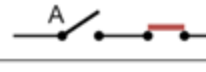
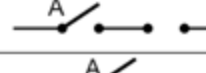
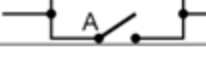
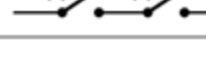
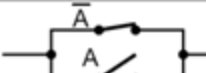
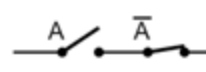
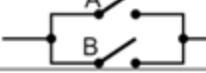
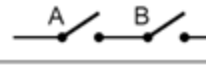
Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\bar{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

- Example (complex →simplified)

$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra


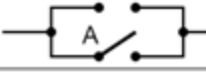
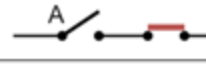
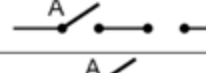
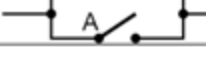
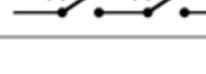
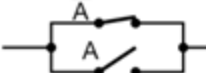
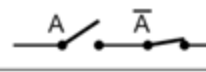
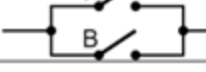
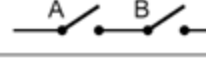
“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

- Example (complex →simplified)

$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$

$$F = AC(\bar{B} + B) + C\bar{D} + CE + D\bar{D} + DE$$

Expand by applying the Distributive Law

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”











- Example (complex →simplified)

$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$

$$F = AC(\bar{B} + B) + C\bar{D} + CE + \boxed{1} + DE$$

$$F = AC + C\bar{D} + CE + DE$$

Applying the Complement Law

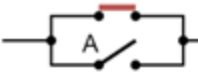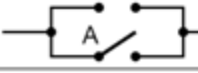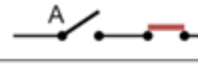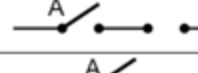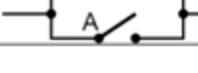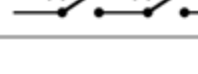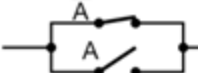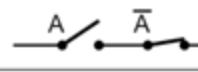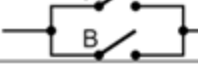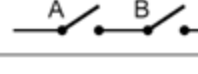Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
NOT $\bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

- Example (complex →simplified)

$$\begin{aligned}
 F &= A\bar{B}C + ABC + (C + D)(\bar{D} + E) \\
 F &= AC(\bar{B} + B) + C\bar{D} + CE + D\bar{D} + DE \\
 F &= AC + C\bar{D} + CE + DE \\
 F &= C(A + \bar{D} + E) + DE
 \end{aligned}$$

Factorise by applying the Distributive Law


Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

 - Example (complex →simplified)

$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$
$$F = AC(\bar{B} + B) + C\bar{D} + CE + D\bar{D} + DE$$
$$F = AC + C\bar{D} + CE + DE$$
$$F = C(A + \bar{D} + E) + DE$$




Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

 - Example (complex →simplified)

$$\begin{aligned} F &= A\bar{B}C + ABC + (C + D)(\bar{D} + E) \\ F &= AC(\bar{B} + B) + C\bar{D} + CE + D\bar{D} + DE \\ F &= AC + C\bar{D} + CE + DE \\ F &= C(A + \bar{D} + E) + DE \end{aligned}$$




Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

 - Example (complex → simplified)

$$\begin{aligned}
 F &= A\bar{B}C + ABC + (C + D)(\bar{D} + E) \\
 F &= AC(\bar{B} + B) + C\bar{D} + CE + D\bar{D} + DE \\
 F &= AC + C\bar{D} + CE + DE \\
 F &= C(A + \bar{D} + E) + DE
 \end{aligned}$$




Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (open) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

“Used to simplify Boolean expressions and reduce the number of logic gates needed in a circuit ”

 - Example (complex →simplified)


$$F = A\bar{B}C + ABC + (C + D)(\bar{D} + E)$$
$$F = AC(\bar{B} + B) + C\bar{D} + CE + D\bar{D} + DE$$
$$F = AC + C\bar{D} + CE + DE$$
$$F = C(A + \bar{D} + E) + DE$$



Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\overline{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Laws of Boolean Algebra

- Example (complex →simplified)

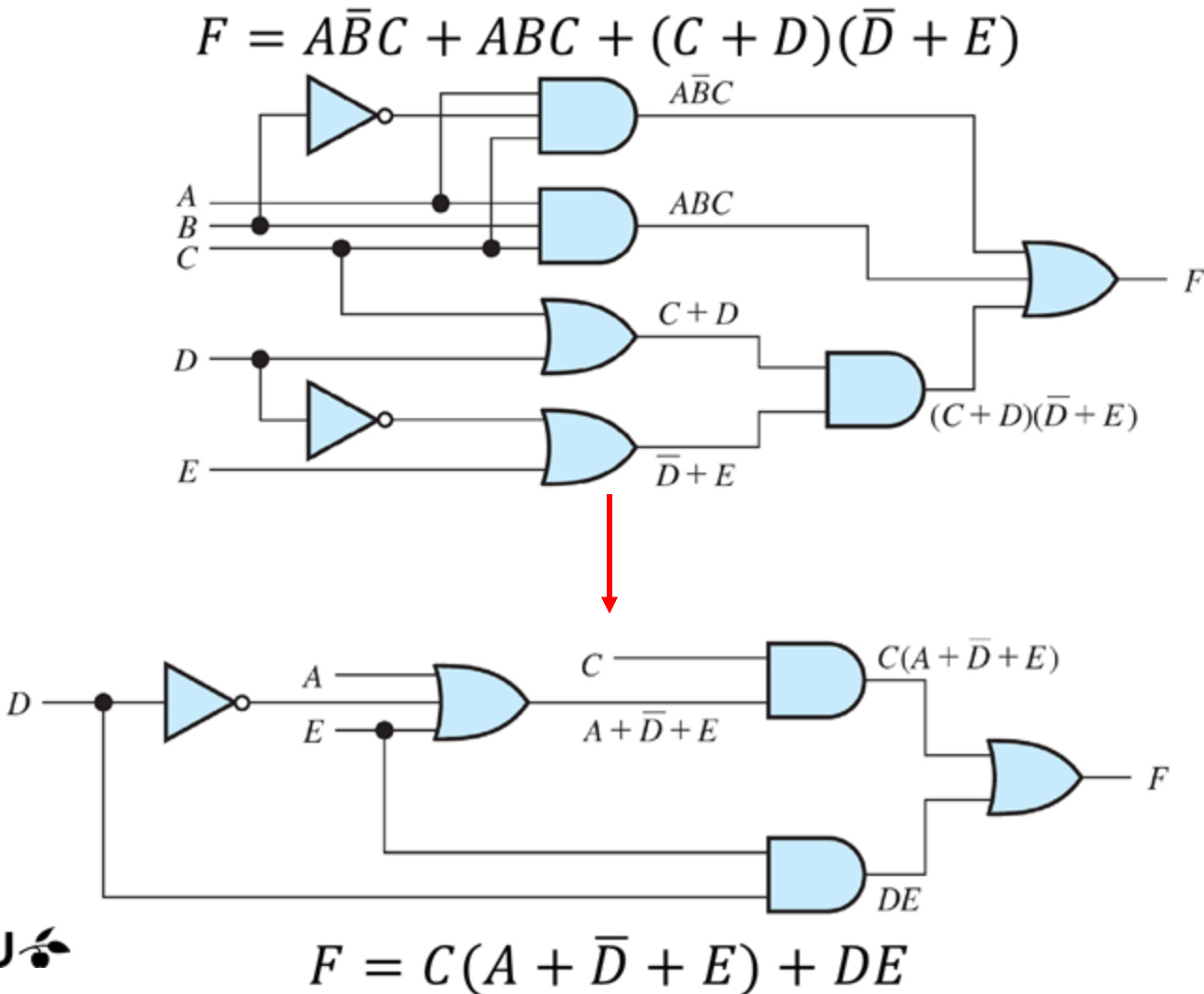

Boolean Expression	Description	Equivalent Switching Circuit	Boolean Law
$A+1=1$	A parallel to 1 (close) equals "CLOSED"		Annulment
$A+0=A$	A parallel to 0 (open) equals "A"		Identity
$A.1=A$	A in series to 1 (close) equals "A"		Identity
$A.0=0$	A in series to 0 (close) equals "OPEN"		Annulment
$A+A=A$	A parallel with itself equals "A"		Idempotent
$A.A=A$	A in series with itself equals "A"		Idempotent
$\text{NOT } \bar{A}=A$	NOT NOT A (double negation) equals "A"		Double Negation
$A+\bar{A}=1$	A parallel to NOT A equals "CLOSED"		Complement
$A.\bar{A}=0$	A in series with NOT A equals "OPEN"		Complement
$A+B=B+A$	A in parallel to B equals B in parallel to A		Commutative
$A.B=B.A$	A in series with B equals B in series with A		Commutative
$\bar{A+B}=\bar{A}.\bar{B}$	Invert and replace OR with AND		De Morgan's Theorem
$\overline{A.B}=\bar{A}+\bar{B}$	Invert and replace AND with OR		De Morgan's Theorem

Portfolio / Lab work